

ARCHIVE 2011

SIGNAL AND POWER INTEGRITY IN THE TEST INTERFACE

by

Jason Mroczkowski

RF Engineering and Product Manager
Multitest Electronic Systems, Inc.

Ryan Satrom

Signal Integrity Engineer
Multitest Electronic Systems, Inc.

ABSTRACT

The instructors for the Tutorial are Jason Mroczkowski & Ryan Satrom of Multitest Electronic Systems, Inc. Both are well known in the socket industry for their high frequency modeling, analysis and design expertise. In this tutorial they'll deliver a comprehensive Tutorial focused specifically on ATE hardware.

This tutorial will expose the audience to the real world implications of designing test hardware to meet various signal integrity and power integrity needs. The tutorial will start by defining the terminology for analog and digital products. The tutorial will move on to present a range of past problematic designs showing real examples of signal and power integrity failures. Armed with a common terminology and previous experience, the tutorial then moves into its main section of providing the attendees with methods to design hardware to meet both the power and signal integrity specifications. Topics ranging from S-parameters, impedance targets, crosstalk, capacitor and inductor fundamentals, measurement equipment, modeling equipment and hardware selection will all be presented during the tutorial.

COPYRIGHT NOTICE

The papers in this publication comprise the pre-workshop Proceedings of the 2011 BiTS Workshop. They reflect the authors' opinions and are reproduced here as they are planned to be presented at the 2011 BiTS Workshop. Updates from this version of the papers may occur in the version that is actually presented at the BiTS Workshop. The inclusion of the papers in this publication does not constitute an endorsement by the BiTS Workshop, the sponsors, BiTS Workshop LLC, or the authors.

There is NO copyright protection claimed by this publication. However, each presentation is the work of the authors and their respective companies: as such, it is strongly encouraged that any use reflect proper acknowledgement to the appropriate source. Any questions regarding the use of any materials presented should be directed to the author/s or their companies.

The BiTS logo and 'Burn-in & Test Socket Workshop' are trademarks of BiTS Workshop, LLC.

Signal and Power Integrity in the Test Interface

Jason Mroczkowski, Ryan Satrom
Multitest



2011 BiTS Workshop
March 6 - 9, 2011



About Multitest economy through technology



- > Multitest is a global one-stop supplier for leading test equipment at best cost of test.
- > The Dover group and Multitest's financial strength assure a long-term partnership.
- > Decades of experience result in comprehensive understanding of the industry.


Innovative Solutions



- test handlers for
 - small packages down to 2x2 mm
 - high parallel test
 - MEMS test
 - tri-temp test



 - contactors for
 - RF to 40GHz
 - Kelvin testing incl. BGAs / WLCSP
 - for pitches down to 0.25 mm / wafer-level packages



- boards for
 - RF test applications
 - fine pitch IC test
 - burn-in test

3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

3

Semiconductor Industry

- Semiconductor market led by:
 - Consumer products
 - iPad, smartphones, netbooks, convenience products
 - Green Energy
 - communications, appliances, transportation, industrial
- “More than Moore”
 - SOP, SIP, 3D packaging
 - Parallelism has allowed faster processing than Moore’s Law
- 8% annual frequency growth rate
- 4% annual supply voltage reduction rate

Data courtesy of New Venture Research 2010 and ITRS 2010

3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

4

Semiconductor Device Trends

- Microprocessors (MPU)
 - Highest revenue semiconductor device
 - Flip-Chip BGA moving toward FBGA
 - Most technological advancements
 - Up to 3.5GHz
 - High Power (~150A)
- Memory
 - Second highest revenue device
 - DDR3 up to 2Ghz
 - DDR4, XDR up to 4GHz
 - FBGA's shifting toward WLP
- Logic
 - FPGA, ASIC, PLDs (largest dies)
 - Flip-Chip BGA (up to ~2000)
 - 25-32 Gbps next Gen
 - Analog
 - Wireless, 4G, 802n, GSM, etc.
 - Smaller packaging QFN, WLP
 - High electrical performance
 - Consumer up to 6GHz
 - Satellite ~30GHz
 - Automotive up to 77GHz

Data courtesy of New Venture Research 2010 and ITRS 2010

3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

5

Semiconductor Packaging Trends

- 0.4mm pitch FBGA's to increase to 20% BGA market by 2015
- Leadless Packages falling from 50% to 40% market by 2015
- FBGA has largest increase and SO largest decrease through 2015
- Drive toward smaller more integrated devices with similar to or better electrical performance creates both signal integrity and power delivery concerns

Data courtesy of New Venture Research 2010 and ITRS 2010

3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

6

Agenda

- Signal Integrity Concepts
- Signal Integrity in the Test Interface
- Power Integrity in the Test Interface

3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

7

Signal Integrity Concepts

3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

8

Signal Integrity Concepts Overview

- What is Signal Integrity?
- Inductance and Capacitance
- Insertion Loss and Return Loss
- S-Parameters
- Impedance
- TDR
- Differential Signals
- Analog-to-Digital Conversions
- Eye Diagrams
- Simulation Techniques

3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

9

What is Signal Integrity?

My working definition:

Signal Integrity is the quality of an electrical signal when the wavelength approaches the size of the signal path

3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

10

Inductance and Capacitance

- Inductance defines the amount of voltage induced when an AC current travels through a component

Time Domain

$$V = L \frac{di}{dt}$$

Frequency Domain

$$Z_L = 2\pi fL$$

- Capacitance is the ability to store charge between two conductors

Time Domain

$$i = C \frac{dv}{dt}$$

Frequency Domain

$$Z_C = \frac{1}{2\pi fC}$$

3/2011


BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

11

Insertion Loss and Return Loss

Insertion Loss

 - Measures Signal Transmission
- Ratio: Transmitted/Input
- S-Parameters: S_{12} , S_{21}
- Specified at -1dB, -3dB



Return Loss

- Measures Signal Reflection
- Ratio: Reflected/Input
- S-Parameters: S_{11} , S_{22}
- Specified at -10dB, -20dB



3/2011


BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

12

S-Parameters

The incident signal:

 - Transmits through structure (S_{12} , S_{21})
 - Insertion Loss
- Reflects back to source (S_{11} , S_{22})
 - Return Loss
 - Impedance
- Absorbs within structure
 - Conductor Loss, Dielectric Loss



S-Parameters models include:

- Information on transmission and reflection for all relevant frequencies
- All necessary information to describe performance

3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

13

Impedance

- Impedance:
 - The relationship between the inductance and the capacitance of a signal path
 - Describes the amount of reflections seen throughout an interface
 - Matched impedance throughout the interface minimizes loss and reflections
 - Focus for signal integrity is instantaneous impedance
- Equation for instantaneous impedance:

$$Z = \sqrt{\frac{L}{C}}$$


3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

14

Impedance

- Two cases: $Z_{SRC} = Z_{LOAD}$, $Z_{SRC} \neq Z_{LOAD}$
- For $Z_{SRC} = Z_{LOAD}$:
 - Interface designed to match impedance throughout interface
 - Most common impedance is 50Ω single-ended (100Ω differential)
- For $Z_{SRC} \neq Z_{LOAD}$:
 - Optimal performance requires interface tuning
 - Tuning optimizes performance within specific frequency band
 - Tuning is achieved by placing inductors and/or capacitors in path**

 

**See "Tuning a PCB/Contactor to Your Device", Ryan Satrom, BiTS 2009.



3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

15


Fluid Flow Analogy

  - Impedance change similar to pipe diameter changing
- Optimal design occurs when pipe diameter/impedance remains constant throughout system



Non-Ideal

Ideal

 


3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

16

Time Domain Reflectometry (TDR)

 - A method for measuring the impedance through an interface
- Can be mathematically derived from S-Parameters
- Used to see inside the structure
- Magnitude of discontinuities depends on rise time of signal
 - Faster rise-time → Larger impact from discontinuity
 - Slower rise-time → Smaller impact from discontinuity



3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

17

Differential Signaling

- Method for data transfer of two complementary signals



- Result is the voltage difference between signals:

$$V_{OUT(DIFF)} = V_{OUT1} - V_{OUT2}$$

- Simplified equation for differential impedance:

$$Z_{DIFF} = Z_{11} + Z_{22} - 2 \times Z_{12}$$

$$Z_{DIFF} = 2 \times Z_0 - 2 \times Z_{12}$$

3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

18

Differential Signals

Advantages

- Reduces Simultaneous Switching Output (SSO) Noise
 - SSO is caused by multiple signals changing the same direction simultaneously
 - Complementary signal changes cancel out, reducing total noise
- Noise Immunity
 - Noise reaching both lines is cancelled out
 - Noise seen on one line has half the impact:
 - Example: 0.1V noise on 1V line
 - Single-Ended: $V_{NOISE} = 0.1V / 1V = 10\%$
 - Differential: $V_{NOISE} = 0.1V / 2V = 5\%$

Disadvantages

- Requires twice the number of signal lines
- Can add EMI if not properly balanced

3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

19

Analog-to-Digital Conversions


Conversions are good as 1st-order assumptions

1) Bandwidth-to-Rise Time

- 10%-90%: Bandwidth(-3dB) $\approx 0.35/TR_{10-90}$
- 20%-80%: Bandwidth(-3dB) $\approx 0.227/TR_{20-80}$

 2) Data Rate-to-Rise Time

- Rise Time $\approx \text{Period}/7 \approx 1/(7 \times \text{Frequency})^{**}$



****Use fundamental frequency, which equals Data Rate / 2**

3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

20

Analog-to-Digital Conversions

- 3) Bandwidth-to-Data Rate
 - Slower data rates require higher harmonic content
 - Higher data rates unable to use higher harmonic content
 - a) 0 – 1 Gb/s:
Bandwidth = 5 x Data Rate = 2.5 * Frequency
 - b) 1 – 5 Gb/s:
Bandwidth = 3 x Data Rate = 1.5 * Frequency
 - c) 5+ Gb/s:
Bandwidth = 1 x Data Rate = 0.5 * Frequency
 - High data rate designs often assume only 1st harmonic
 - Trade-offs made in other areas of design


3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface


21

Harmonics of Digital Signals

 
- Signal output of square wave input based on an interface that passes specific harmonics




1st-Harmonic Only

 

1st, 3rd Harmonics

 

1st, 3rd, 5th Harmonics

 

1st, 3rd, 5th, 7th Harmonics


3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

22

Eye Diagrams

 - Eye Diagrams are graphical displays of data that overlay repeating periods of the same data
- Used to analyze digital signals
- Depicts signal fidelity in time domain
- Become increasingly useful with increased speeds
- Several aspects used to describe performance
 - Eye Height, Eye Width, Jitter, Overshoot, Rise-Time, Fall-Time, Crossing-Time, Intersymbol Interference (ISI)




3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface



23

Simulation Techniques

 - 1) Lumped Element Models (SPICE)
 - Appropriate below ~1 GHz
- 2) Distributed Element Models
 - Highly accurate; only valid for constant cross-section



  - 3) Full 3D Electromagnetic Simulation
 - Required for complex structures such as vias, contactors
 - Most resource intensive, but also most accurate



3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

24

Signal Integrity in the Test Interface



3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

25

SI in the Test Interface Agenda

- PCB Traces
- Vias
- Contactor
- System

  


3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

26

Signal Integrity in the Test Interface

PCB Traces

 

3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

27

General PCB Guidelines

- 1) In general, most loss in test interface is due to the PCB
 - PCB trace length $\approx 4''$ - $16''$
 - Contactor probe length $\approx 0.05''$ - $0.3''$
 - PCB trace length $\gg$ contactor probe length
- 2) PCB loss mainly due to length, not reflections
 - Impedance typically controlled within $\pm 10\%$
 - Reflections are minimized

	PCB	Contactors
Length	Long	Short
Impedance Control	Easy	Difficult

3/2011


BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

28

General PCB Guidelines

 3) Expect more loss in PCB than specifications suggests

- Expect up to 50% more loss in actual PCB
- Tan δ values
 - Typical specifications: 0.002-0.02
 - More representative: 0.008-0.025




3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface


29

General PCB Guidelines

 - Reasons for discrepancy in performance
 - Vendor specifications do not reflect PCB environment
 - Some PCB materials require harder copper for adhesion which increases roughness and loss
 - Etch/material tolerances
 - Dielectric/weave variation



PCB Weave

 

Copper Roughness


3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

30

General PCB Guidelines

 - 4) Doubling trace width improves performance about 30%



	Loss @ 2 GHz
2mil Wide	-5.6 dB
4mil Wide	-4.0 dB
8mil Wide	-2.9 dB
16mil Wide	-2.3 dB
32mil Wide	-2.0 dB

3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

31

General PCB Guidelines

- 5) Trace width for 50Ω microstrip is roughly 2X core thickness
- Example: Core thickness = 8mil → Trace width = 16mil



- 6) Trace width for 50Ω stripline is roughly 1X core thickness
- Example: Core thickness = 8mil → Trace width = 8mil



*See Appendix 1 to see how different variables impact impedance

3/2011



BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

32

General PCB Guidelines

- 7) Microstrip performance about 30% better than stripline
- 8) Soldermask has a negligible impact on signal integrity

	Loss @ 2 GHz	
	4"	12"
Stripline	-0.9 dB	-2.6 dB
Microstrip	-0.7 dB	-2.0 dB
Microstrip w/ Soldermask	-0.7 dB	-2.0 dB

  

*Assumes core thickness is modified to maintain 50Ω impedance

3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

33

Typical PCB Insertion Loss Values

	(-1dB) <u>Stripline</u>	(-1dB) <u>Microstrip</u>
• 2" Trace	3-7 GHz	4-10 GHz
• 4" Trace	1-3 GHz	1.5-4.5 GHz
• 8" Trace	0.4-1.2 GHz	0.6-1.8 GHz
• 16" Trace	0.1-0.4 GHz	0.2-0.7 GHz


3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

34

Signal Integrity in the Test Interface

Vias

 


3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

35

General Via Design Guidelines

 - 1) Place critical signals close to center of the PCB stackup
 - Two medium-sized vias/stubs are better than one small and one large via/stub



3/2011


BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

36

General Via Design Guidelines

2) Place ground via within 1mm of every signal via

 - Example:
 - 0.250" PCB
 - Signal on bottom stripline layer



3/2011


BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

37

General Via Design Guidelines

 3) Backdrill signals above 1GHz

- Signal layer location, via stub are not issues < 1 GHz**
- Example:
 - 0.250" PCB
 - Compares signals on top-half, bottom-half of PCB



**Assumes ground via within 1mm


3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

38

Signal Integrity in the Test Interface

Contactors

 


3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

39

General Contactor Guidelines

 - 1) Most contactors are adequate for sub-1GHz signals
- 2) Performance for differential signals is typically much better than performance of single-ended signals
 - $Z_{\text{CONTACTOR}}$ (Single-Ended) $\gg 50\Omega$
 - $Z_{\text{CONTACTOR}}$ (Differential) $\approx 100\Omega$
 - Z_{DIFF} typically a much closer match than Z_{SE}
- 3) Ground proximity critical for determining performance



Also see Appendix 3 to see how different variables impact contactor impedance

3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

40

General Contactor Guidelines

- 4) Performance is not *Black Magic*
 - Two probes with similar length/diameter will have similar performance
 - Beware of specifications that don't seem to make sense
- 5) Shorter probes are better because they minimize the mismatch
 - If impedance is matched, length is only a very minor issue
- 6) Tuning applications are the exception to the rule
 - Shorter, higher bandwidth probe not always best solution
 - Requires component tuning on PCB to optimize performance**

**Tuning is required when $Z_{\text{SOURCE}} \neq Z_{\text{TERM}}$; See "Tuning a PCB/Contactor to Your Device", Ryan Satrom, BiTS 2009.

3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

41

Typical Contactor Insertion Loss (-1dB)

SINGLE-ENDED ($Z_0=50\Omega$)

- G-S-G (GND SIG GND)** 20-40 GHz
- G-S (GND SIG) 3-12 GHz
- G-S (DIAG) (GND FLOAT SIG) 2-7 GHz
- G-X-S (GND FLOAT SIG) 1.5-5 GHz
- G-X-X-S (GND FLOAT FLOAT SIG) 1-3 GHz

DIFFERENTIAL ($Z_0=100\Omega$)

- S-S (SIG SIG) 15-20 GHz
- G-S-S (GND SIG SIG) 15-20 GHz
- G-S-S-G (GND SIG SIG GND) 15-20 GHz

**GSG is standard datasheet specification, also see Appendix 2 for Return Loss Comparison

3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

42

Typical Contactor Impedance (Ω)

SINGLE-ENDED ($Z_0=50\Omega$)

- G-S-G (GND SIG GND)** 55-65 Ω
- G-S (GND SIG) 70-90 Ω
- G-S (DIAG) (FLOAT SIG) 75-100 Ω
- G-X-S (GND FLOAT SIG) 85-170 Ω
- G-X-X-S (GND FLOAT FLOAT SIG) 110-220 Ω

DIFFERENTIAL ($Z_0=100\Omega$)

- S-S (SIG SIG) 100-110 Ω
- G-S-S (GND SIG SIG) 95-105 Ω
- G-S-S-G (GND SIG SIG GND) 85-100 Ω

3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface


43

Contactor Designs – Changing Dielectric


- The contactor body can be changed to modify the dielectric constant of material

Performance Comparison

Single-Ended

 

Differential

 

3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

44

Contactor Designs – Changing Dielectric

Is it worth modifying dielectric for RF performance?

- **Sometimes** for High-speed single-ended signals
 - Depends on pitch, ground configuration, frequency
 - Difference may be seen above ~2 GHz
 - Choose on case-by-case basis – Performance will just as often degrade as it will improve
- **Rarely** for high-speed differential signals
 - Differential signals typically have good impedance match through contactor

3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

45

Contactor Designs – Coaxial

Strengths


- Optimized impedance
- Improve bandwidth
- Improve crosstalk

Weaknesses

- Mechanical challenges
- Low force probes
- Expense

Performance Comparison

Single-Ended

 


3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

46

Differential

 

Contactor Designs – Coaxial

Is it worth using a coaxial contactor?

- **Sometimes** for High-speed single-ended signals
 - Depends on pitch, ground configuration, frequency
 - Potential benefit may be seen above ~2 GHz
- **Never** for High-speed differential signals
 - Differential signals typically have good impedance match through contactor without coax
 - Differential signals benefit from coupling between complementary signals – Coax removes this benefit



3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

47

Contactor Designs – QFN Grounding

  - Where should ground probes be placed?
- Simulation compares performance as ground probes move further away from signal probe




3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

48

Contactor Designs – QFN Grounding

 - Results show ground probes need to be place as close to periphery as possible





3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

49

Contactor Designs – QFN Grounding

  - Are ground slugs better than ground probes?
- Simulation compares performance with and without ground slug





3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

50

Contactor Designs – QFN Grounding

  - Performance between slug and probes with same spacing is very similar



- However, there are cases where ground slug will provide benefit


3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

51

Contactor Designs – QFP Grounding

 - If device has small ground pad, ground slug can improve performance
 - Ground probe locations will be limited by size of ground pad
 - Ground slugs can get much closer to signal pins





3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

52

Contactor Designs – QFP Grounding

  - Ground slugs
 - Can improve performance through contactor AND through package
 - Brings contactor/package ground reference closer to signals





3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

53

Contactor Performance w/ PCB Launch

  - Launch reduces bandwidth due to three variables:
 - 90° transition
 - Via length
 - Stub length (if not backdrilled)



- Example
 - Compare different layers, ground configurations on 0.187" PCB

3/2011



BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

54

Contactor Performance w/ PCB Launch

G-S (GND SIG) Configuration

	<u>-1dB</u>	<u>-3dB</u>
Contactor Only	5.5 GHz	24 GHz
Contactor/Launch (Backdrill)	3-4.5 GHz	7-8 GHz
Contactor/Launch (No Backdrill)	2.7 GHz	3.5-5.5 GHz

  

3/2011



BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

55

Contactor Performance w/ PCB Launch

G-S-G (GND SIG GND) Configuration

	<u>-1dB</u>	<u>-3dB</u>
Contactor Only	21.5 GHz	27 GHz
Contactor/Launch (Backdrill)	10 GHz	25 GHz
Contactor/Launch (No Backdrill)	3.5-6 GHz	5-12 GHz

  

3/2011



BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

56

Contactor Performance w/ PCB Launch

G-S-S-G (GND SIG SIG GND) Configuration

	<u>-1dB</u>	<u>-3dB</u>
Contactor Only	16 GHz	28 GHz
Contactor/Launch (Backdrill)	13-21 GHz	26-28 GHz
Contactor/Launch (No Backdrill)	3-10 GHz	5-13 GHz

  


3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

57

Signal Integrity in the Test Interface

System

 

3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

58

System Rules of Thumb

- What is the loss budget for a typical system?
- Industry rule of thumb is -3dB:
 - 1dB → Contactor
 - + -1dB → PCB
 - + -1dB → Everything else**
 - 3dB → System
- -3dB is a VERY rough approximation
- Actual loss can be much more, up to -20dB
- Several variables dictate actual requirements

**includes connectors, cabling, launches


3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

59

Digital Applications

 - -3dB rule of thumb is insufficient
- Some applications can handle up to -20dB
- Example:
 - View 10GB/s eye diagrams for different interfaces
 - Compare 1dB, 3dB, 10dB, 20dB at fundamental



3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface


60

Digital Applications

- Results

-1dB

EYE _{HEIGHT}	865 mV
EYE _{WIDTH}	99 ps
JITTER _{Rp-p}	1 ps
T _{RISE-OUT}	26 ps

 


-3dB

EYE _{HEIGHT}	624 mV
EYE _{WIDTH}	95 ps
JITTER _{Rp-p}	3 ps
T _{RISE-OUT}	33 ps




-10dB

EYE _{HEIGHT}	41 mV
EYE _{WIDTH}	57 ps
JITTER _{Rp-p}	26 ps
T _{RISE-OUT}	59 ps

 

-20dB

EYE _{HEIGHT}	N/A
EYE _{WIDTH}	N/A
JITTER _{Rp-p}	N/A
T _{RISE-OUT}	N/A

 

3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

61

Digital Applications

- Recovering data
 - It is possible to recover data with significant loss
 - Data often recovered using pre-emphasis or equalization
 - Pre-emphasis → Modifies content at the output
 - Equalization → Modifies content at the input
- Linear loss (due to PCB length) is much easier to offset than non-linear loss (due to discontinuities)
 - Return loss quantifies reflections and can be more critical than insertion loss


3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

62

Analog Applications

 - -3dB rule of thumb is insufficient
- Some applications can handle up to -10dB
- Concern is narrowband (one specific frequency range) instead of broadband
- Tuning is often required for analog signals to optimize performance






3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

63

Realistic Loss Expectations

   - Simulation Example
Tester Via → PCB Trace → PCB/Contactor



- Variables:

Tester Via
Backdrill (Y/N)

PCB Trace
uStrip/Stripline
Trace Width
PCB Material

PCB/Contactor
Backdrill (Y/N)
Signal Layer
 $Z_{\text{CONTACTOR}}$

3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

64

Realistic Loss Expectations

- Simulation Example Results
Tester Via → PCB Trace → PCB/Contactor
(-3dB)
- System w/ 2" Trace 3-20 GHz
- System w/ 4" Trace 2.5-10 GHz
- System w/ 8" Trace 1.5-6 GHz
- System w/ 12" Trace 1-4 GHz
- System w/ 16" Trace 0.7-3 GHz

3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

65

Realistic Loss Expectations

- Simulation Example Results
 - Variables that impact bandwidth
- | | Lower S_{21} | Higher S_{21} |
|--------------------------|------------------|-----------------|
| • Backdrill | No | Yes |
| • Topology | Stripline | Microstrip |
| • Trace Width | Narrow | Wide |
| • PCB Material | FR4-type | Exotic |
| • Signal Layer | Close to Surface | Close to Center |
| • $Z_{\text{CONTACTOR}}$ | GS | GSG, GSSG |


3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

66

Source of Loss

- Example: 16" System**

 

Loss	<u>1GHz</u>	<u>5GHz</u>
• PCB Trace	2.3dB (95%)	8.3dB (85-95%)
• Vias/Contactor	0.1-0.2dB (5%)	0.5-1.5dB (5-15%)
• Total	2.4-2.5dB	8.8-9.8dB

****See Appendix 4 for comparisons with other trace lengths**

3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

67

Power Integrity in the Test Interface

3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

68

PDN Agenda

- Introduction to Power Delivery Network
- Key PDN Concepts
- PDN Example

3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

69

Introduction to the PDN

- Goal of Power Delivery Network (PDN)
 - Provide constant voltage to DUT in high di/dt environment
- Requirement of PDN
 - Maintain low impedance path from tester to DUT across all operating frequencies of device


Tester (Voltage
Regulator Module)



Contactor (Probes)



PCB (Planes/capacitors)

 

DUT (Package/die)


3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

70

Introduction to the PDN

 - Good PDN design minimizes noise on the power and ground rails
- Problems caused by poor PDN:
 - Voltage droop
 - Rail collapse
 - Voltage spikes
 - Ground bounce
 - Simultaneous Switching Noise
 - Power-supply-induced jitter




3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

71

Introduction to the PDN

 - IC Power Supply Voltage
 - Yesterday 5V
 - Today 1V (5x reduction)
- Typical Supply Ripple allowed
 - Yesterday 5-10%
 - Today 0.5% (up to 20x reduction)
- Current requirements
 - Yesterday 10A
 - Today 150A (15x increase)
- Z_{TARGET} requirements
 - Yesterday 100m Ω
 - Today 1m Ω (100x reduction)



Year	Power (W)	Vdd (V)	Idd (A)
2010	146	0.97	151
2011	161	0.93	173
2012	158	0.90	176
2013	149	0.87	171
2014	152	0.84	181
2015	143	0.81	177
2016	130	0.78	167

Data courtesy of ITRS 2010


3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface


72

Considerations for ATE Environment

 - High-layer-count PCB requires long vias
 - Increases distance to capacitors
- Large PCB
 - Increases distance to power supply and capacitors
- High-density PCB
 - Routing requirements limit space for capacitors



 1 mm pitch 7396 pin BGA
46 electrical layers



1 mm pitch 1924 pin BGA
1900 components, 592 relays

3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

73

Considerations for ATE Environment

- Contactor
 - Increases distance to capacitors
- Limited specifications
 - Detailed device power consumption unavailable
 - Requires approximations to be made for PDN design
- Wide range of devices
 - Requires generic rules and conservative design




3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

74

Path of Power Delivery Network

 


Voltage Regulator Module (VRM) Power/Ground Planes




TOP METAL	6 MIL (0.15MM)
POWER LAYER	3 MIL (0.07MM)
GROUND LAYER	6 MIL (0.15MM)
SIGNAL LAYER	6 MIL (0.15MM)
GROUND LAYER	6 MIL (0.15MM)
BOTTOM METAL	6 MIL (0.15MM)

Contactor

 

Bypass
Capacitors


Bulk
Capacitors

 

Package /Capacitors



Die

 

3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

75

Impedance in Power Delivery Network

SI Impedance


Ideal $Z = 50\Omega$

Ideal $Z \rightarrow$ high bandwidth

Instantaneous impedance

Time domain

$$Z = \sqrt{\frac{L}{C}}$$

 

PDN Impedance


Ideal $Z \approx 0\Omega$

Ideal $Z \rightarrow$ constant voltage

Aggregate impedance response

Frequency domain

$$Z = R + 2\pi fL + \frac{1}{2\pi fC}$$

 


3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

76

Understanding the PDN Impedance

 - Lowest path to ground will vary based on frequency



Signal Frequency

Impedance

• 250 MHz	15Ω	2Ω	0.5Ω
• 80 MHz	5Ω	0.5Ω	2Ω
• 30 kHz	0.5Ω	53Ω	5300Ω

3/2011


BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

77

Capacitance in PDN

- Ideal capacitors (C) have linear frequency response
- Real capacitors include parasitic inductance and resistance
 - Equivalent Series Inductance (ESL)
 - Inductance of path from the DUT to the capacitor
 - Limits the useful frequency range of capacitor
 - Equivalent Series Resistance (ESR)
 - Dampens the impedance peaks
 - Minimum impedance of capacitor

$$Z = R + 2\pi fL + \frac{1}{2\pi fC}$$

 

3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

78

Capacitance in PDN

- Capacitors used to provide low impedance (AC) from power to ground
- Multiple capacitors placed throughout PCB to cover all frequencies


Large caps (Bulk)

High C and High L
Low Z at low frequency

Small Caps (Bypass)

Low C and Low L
Low Z at high frequency

$$Z = R + 2\pi fL + \frac{1}{2\pi fC}$$

 

3/2011


BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

79

Inductance in PDN

- Inductance of single probe/via/trace is not practical
- Equation for loop inductance:
 
$$L_{\text{LOOP}} = L_{\text{SELF-SIG}} + L_{\text{SELF-RTN}} - 2 \times L_{\text{MUTUAL}}$$
- L_{MUTUAL} : Mutual Inductance between signal path and return path



See also "Determining Inductance in Contactors", Ryan Satrom, BiTS 2007

3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

80

Inductance in PDN

ESL includes the path from the DUT to the capacitor

- 1) Die/Package
- 2) Contactor
- 3) DUT Vias
- 4) Planes
- 5) Vias/Capacitor



- PCB Inductance is based on:
 - Cap to DUT distance
 - Power/Ground core thickness
 - Power plane geometry
 - Via length
- Contactor Inductance is based on:
 - Probe length
 - Probe diameter
 - Proximity of power pins to ground pins
 - Number of power ground pairs

3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

81

Inductance in PDN


- In BGAs, inductance minimized by alternating powers and grounds in layout.
- Typical power/ground to signal ratio 1:1
- Grouping all grounds together yields higher inductance
- Grounds in center have no impact on improving inductance

RED = VDD1 BLUE = VDD2 GREEN = GND WHITE = N/C

POOR LAYOUT



GOOD LAYOUT

 

3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

82

Minimizing the Inductance

- Use short, low inductance contactor
 - e.g. Gemini™, Mercury™ contactors
- Minimize area of current loops
 - Use low ESL capacitors
 - e.g. X2Y®, Capacitor Arrays
 - Place power/ground vias as close to each other as possible
 - Place bypass capacitors as close to DUT as possible
 - Capacitor interposers (e.g. 3M™, AVX™)
- Maximize width of conductors
 - Wide traces, wide planes
- Minimize spacing between ground and power planes
 - Thin-core dielectrics (e.g. Faradflex™, ZBC®, Integra™)
- Use multiple parallel paths, pairs of vias, pairs of planes
- Alternate polarity of capacitor vias



3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

83

Defining the Target Impedance

- Required impedance is application-specific
 - Every device has its own unique current profile
 - Difficult to apply a standard to PDN design
- Device specification dependent
 - Impedance calculated from datasheet specifications
- Z_{TARGET} approximated using one of the following:
 - Transient currents
 - Power consumption
 - Simulated IC models
 - Equation for target impedance using transient current:

$$Z_{\text{TARGET}} = V_{\text{CC}} \times V_{\text{RIPPLE}}(\%) / I_{\text{TRANSIENT}} \quad [\text{where } I_{\text{TRANSIENT}} = \frac{1}{2} I_{\text{CCMAX}}]$$


Symbol	Parameter	Minimum	Typical	Maximum	Unit
V_{CC}	Power supply voltage	7.6	8.0	8.4	V
I_{CC}	Power supply current		190	250	mA

3/2011


BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

84

Impedance Profile of PDN

 

 1. VRM (sub-10kHz)
2. Bulk capacitors (1kHz - 5MHz)
3. Bypass capacitors (1MHz - 100MHz)
4. Package (10MHz - 300MHz)
5. On-die decoupling (100MHz+)



Aggregate Response



3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

85

PDN Example

  - Example: 1000-pin BGA 1mm pitch
 - $V_{CC} = 1V$ (5% ripple), $I_{MAX} = 100A$
- Pin Assignment Approximations:
 - 25% Power, 25% Ground, 25% Status I/O, 25% HS I/O
- Use one voltage supply – 250 PWR, 250 GND pins*
- Solving for the required impedance
 - $Z_{TARGET} = V_{CC} \times V_{RIPPLE}(\%) / I_{TRANSIENT}$
 - $Z_{TARGET} = 1V \times 0.05 / 50A = 1m\Omega$



*Most large BGAs have multiple power supplies. One supply is used to simplify example.


3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

86

PDN Example

 - Design Strategy:
 - Define Z_{PDN} independently across each PDN region
 - Determine the aggregate response including each successive region
 - Optimize Z_{PDN} to meet Z_{TARGET} of 1m Ω across all frequencies




3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

87

PDN Region #1: VRM

 

- VRM
 - Provides the power to the DUT
 - Senses voltage at DUT and changes current to maintain constant DC voltage
 - Effective for very low frequencies
 - Typical value for $L = 25\text{-}50\text{nH}$
- Performance limited by the inductance:

$$Z_L = 2\pi f_{MAX} L$$
- Assuming $L = 30\text{nH}$, Z_{TARGET} reached at:


$$f_{MAX} = \frac{Z_{TARGET}}{2\pi * L_{VRM}} = \frac{1\text{m}\Omega}{2\pi * 30\text{nH}} = 5\text{kHz}$$

3/2011


BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

88

PDN Region #1: VRM

 

 - Plot shows impedance below Z_{TARGET} up to 5kHz




3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

89

PDN Region #2: Bulk Capacitors

 

- Bulk capacitance must keep impedance below Z_{TARGET} beyond 5kHz
- Bulk capacitor ESR typically 2-100mΩ
- Equation for impedance of a capacitor:

$$Z_C = \frac{1}{2\pi f_{MAX} C}$$

- Using $f=5\text{kHz}$ and $Z_{TARGET} = 1\text{m}\Omega$

$$C_{BULK} > \frac{1}{Z_{TARGET} * 2\pi * 5\text{kHz}} = 30,000 \mu\text{F}$$


- Total C_{BULK} will be split up between multiple capacitors with value of C_{BULK}/n , where $n = \#$ of capacitors

3/2011



BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

90

PDN Region #2: Bulk Capacitors

 

  - Results for $C_{BULK}=30,000\mu F$ creates peak at 5kHz
- Peak reduced by increasing capacitance to 75,000 μF and ESR from 2m Ω to 5m Ω
- f_{MAX} is determined by inductance from DUT to bulk capacitors




3/2011


BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

91

PDN Region #2: Bulk Capacitors

 

 - Typical values of L_{BULK} are 1nH-20nH
- Results in f_{MAX} from 80kHz-1.4MHz
- 5nH (blue) will be used for L_{BULK} ($f_{MAX} = 300kHz$)




3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

92

PDN Region #3: Bypass/PCB/Contactor

 

- Bypass capacitance must provide low impedance path beyond 300kHz
- Using $f=300\text{kHz}$ and $Z_{\text{TARGET}} = 1\text{m}\Omega$, solving for C:

$$C_{\text{BYPASS}} > \frac{1}{Z_{\text{TARGET}} * 2\pi * 300\text{kHz}} = 500\mu\text{F}$$

- Total C_{BYPASS} will be split up between hundreds of capacitors with value of C_{BYPASS}/n , where $n = \#$ of capacitors


3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

93

PDN Region #3: Bypass/PCB/Contactor

 - One capacitor per pin (250 capacitors total)
- C_{BYPASS} set to $1000\mu\text{F}$ to minimize impedance peak ($250 \times 4\mu\text{F}$)
- L_{BYPASS} varies from 2.5nH - 7.5nH (3nH is used)
- Plot shows impact from varying contactor inductance
- Results in f_{MAX} from 6MHz - 16MHz



3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface


94

PDN Region #3: Bypass/PCB/Contactor

- f_{MAX} of bypass path is maximum frequency that the ATE interface can keep impedance below Z_{TARGET}
- f_{MAX} is determined by inductance of path from DUT to bypass capacitors (L_{BYPASS})

$$Z_{BYPASS} = 2\pi f_{MAX} L_{BYPASS}$$

 - Typical f_{MAX} ranges from 1-100MHz
- Contactor inductance only impacts PDN up to $\sim f_{MAX}$




3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface


95

PDN Region #3: Bypass/PCB/Contactor

 

- PCB Planes
 - The capacitance of the PCB planes will interact with the parallel loop inductance of the bypass network to create a resonance
 
$$f_{RES} = \frac{1}{2\pi * \sqrt{L_{BYPASS} * C_{PLANES}}}$$




3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

96


PDN Region #4: Package

 

- The package inductance limits f_{MAX} of the ATE interface
- Some packages can add capacitors to help increase f_{MAX}



Package Caps

 


- Typical inductance values (per power/ground pair)
 - Leaded packages ~3-7nH
 - Chip-scale packages ~1-3nH
 - BGA packages (wire-bond) ~ 1-5nH
 - BGA packages (flip-chip) ~0.1-0.5nH

3/2011


BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

97

PDN Region #4: Package

 

- Package Inductance
 - Flip-Chip technology, $L = 0.1\text{nH}$
 - $L_{PKG} = 0.1\text{nH}/250 \text{ power pins} = 0.4\text{pH}$
- Package Capacitors
 - 10 capacitors
 - $C_{PKG} = 1000\text{nF} \times 10 \text{ capacitors} = 10\mu\text{F}$
 - $L_{PKG-CAP} = 50\text{pH} / 10 \text{ capacitors} = 5\text{pH}$
- 1st order approximation for f_{MAX} of Package:
 - $Z_{PDN} < 2\pi \times (L_{PKG} + L_{PKG-CAP}) \times f_{MAX}$
 - $f_{MAX} \approx Z_{PDN} / (2\pi (L_{PKG} + L_{PKG-CAP})) \approx 0.001 / (2\pi \times 5.4\text{pH})$
 - $f_{MAX} \approx 30\text{MHz}$

 


3/2011



BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

98

PDN Region #4: Package

 

  - Results create peak above Z_{TARGET}
- Peak can be reduced by:
 - Decreasing L_{BYPASS} (set at 3nH)
 - Increasing C_{PKG} (from 10 x 1 μ F to 25 x 1 μ F)
 - Increasing R_{PKG} (from 1m Ω to 5m Ω)




3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

99

PDN Region #5: Die

 


- Remaining decoupling must be accomplished by the capacitance on the die
- On-die capacitance comes from three areas:
 - Power ground grid
 - Gate capacitance due to millions of transistors
 - Thin oxide capacitance in silicon

3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

100

PDN Region #5: Die

 

- On-die capacitance can be approximated based on technology*:

Channel Length	Capacitance
130nm	130nF/cm ²
65nm	260nF/cm ²
50nm	340nF/cm ²
32nm	520nF/cm ²
22nm	770nF/cm ²

- Assume DIE_{SIZE} = 2cm²**
- Technology → 32nm**

$$C_{DIE} = \frac{520nF}{cm^2} * 2cm^2 = 1.04\mu F$$

*See "Signal and Power Integrity – Simplified", Eric Bogatin, p677


**Reflects current BGA technology

3/2011


BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

101

PDN Region #5: Die

 

 - Results create additional peak above Z_{TARGET}
- Peak can be reduced by:
 - Decreasing L_{PKG}
 - Increasing C_{DIE}




3/2011


BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

102

PDN System Summary

 

 - Plot overlay shows the frequencies where each region has impact



3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

103

PDN Example Limitations

- This PDN design results in impedance higher than Z_{TARGET} for frequencies in the 100MHz range
 - The only way to meet the target impedance is to decrease inductance (L_{BYPASS} , L_{PKG}) or increase capacitance (C_{PKG} , C_{DIE})
 - Design may cause problems if device has a large number of signals in the 100MHz range
 - Impedance target can be very difficult to meet across all frequencies

3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

104

PDN Conclusions

- Power Delivery Network design is complicated
- Devices have unique impedance profile requirements
- The task of accurately modeling the PDN is challenging
- PCB, contactor, package and die all play a role in the PDN
- Understanding how each component impacts the overall performance of the PDN is required to design a quality system
- The focus on power integrity will increase in the coming years

3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

105

Recommended Resources

- “Power Integrity Modeling and Design for Semiconductors and Systems”, Ege Engin and Madhavan Swaminathan, 2007.
- “Signal and Power Integrity – Simplified”, Eric Bogatin, 2nd edition, 2009.

3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

106

Appendix 1 – Modifying PCB Impedance

- There are several factors that impact impedance
- In PCB Traces: Z

- ↑ Trace Width ↓
- ↑ Dielectric Thickness ↑
- ↑ Trace Thickness ↓ **
- ↑ Dielectric constant of material ↓
- ↑ Trace Length ↔

**Minor impact

3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

107

Appendix 2 - Contactor Return Loss (-10dB)

SINGLE-ENDED ($Z_0=50\Omega$)

- G-S-G (GND SIG GND) ** 5-25 GHz
- G-S (GND SIG) 2-8 GHz
- G-S (DIAG) (GND FLOAT SIG) 1.5-5 GHz
- G-X-S (GND FLOAT SIG) 1-3.5 GHz
- G-X-X-S (GND FLOAT FLOAT SIG) 0.5-2.5 GHz

DIFFERENTIAL ($Z_0=100\Omega$)

- S-S (SIG SIG) 12-30 GHz
- G-S-S (GND SIG SIG) 12-30 GHz
- G-S-S-G (GND SIG SIG GND) 12-30 GHz

**GSG is standard datasheet specification

3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

108

Appendix 3 - Modifying Contactor Impedance

- There are several factors that impact impedance
- In contactors:

Z

- ↑ Number of adjacent GND pins ↓
- ↑ Pitch ↑
- ↑ Probe Diameter ↓
- ↑ Dielectric constant of material ↓
- ↑ Probe Length ↔


3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

109

Appendix 4 - Source of Loss (4")

- Examples: 4" System

 

- Loss
- | | <u>1GHz</u> | <u>5GHz</u> |
|------------------|--------------------|--------------------|
| • PCB Trace | 0.6dB (75-85%) | 2dB (60-80%) |
| • Vias/Contactor | 0.1-0.2dB (15-25%) | 0.5-1.5dB (20-40%) |
| • Total | 0.7-0.8dB | 2.5-3.5dB |


3/2011

BiTS 2011 Tutorial: Signal and Power Integrity in the Test Interface

110

Appendix 4 - Source of Loss (8")

- Examples: 8" System

 

- Loss

	<u>1GHz</u>	<u>5GHz</u>
• PCB Trace	1.2dB (85-95%)	4dB (75-90%)
• Vias/Contactor	0.1-0.2dB (5-15%)	0.5-1.5dB (10-25%)
• Total	1.3-1.4dB	4.5-5.5dB